 




Introduction to Verilog and SystemVerilog

Saul Rodriguez





OUTLINE


- MOTIVATION
- VERILOG FAMILY
- VERILOG RTL AND SYNTHESIS EXAMPLES
- SYSTEMVERILOG
- FINAL REMARKS

MOTIVATION

- Digital design flows evolve towards high level languages
 - Higher productivity
 - Shorter design and verification time
 - Easy to learn
- VHDL is based on ADA
 - ADA is Strong typed, code safe
 - ADA is not very widely used
- Verilog is based on C
 - C is weak typed
 - C is the most widely spread language
 - C++, Java, C#, Objective C, Pearl, etc.

MOTIVATION

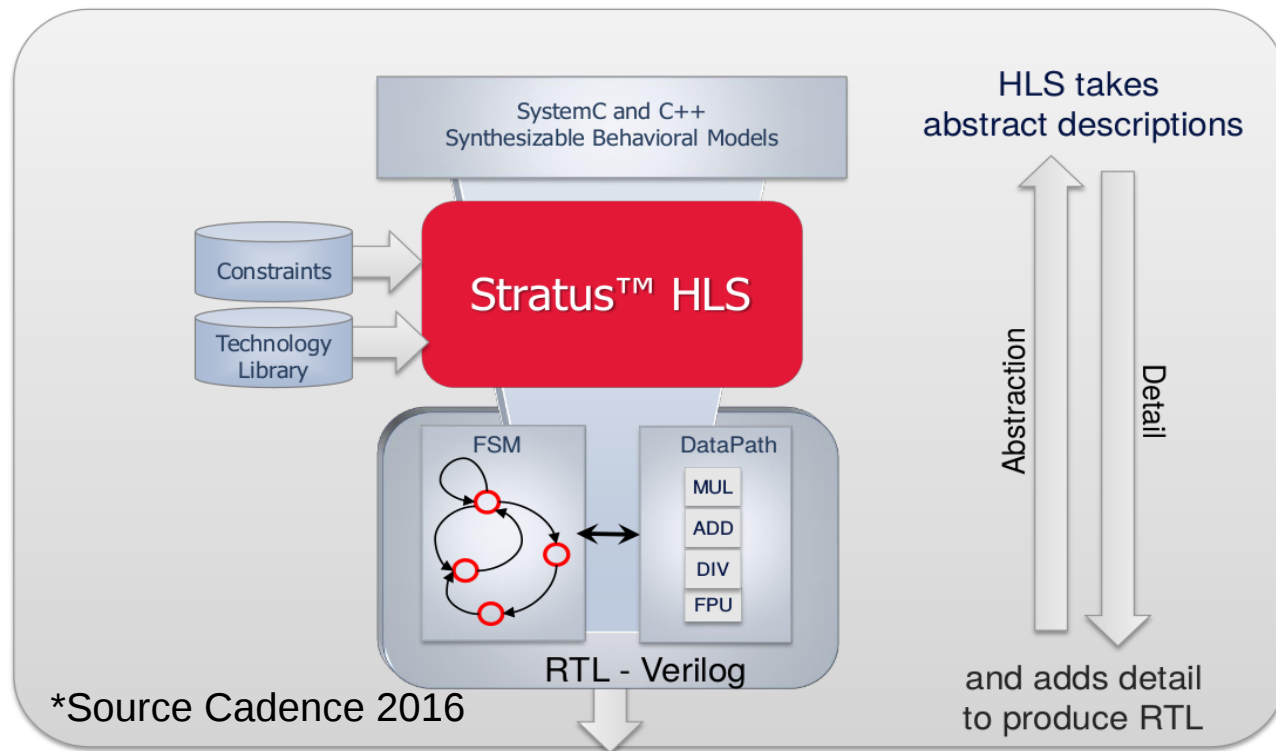- ASIC EDA tools are influenced by a limited number of players that decide what tool you will use.



MOTIVATION

- ASIC Foundries decide which tools are primarily supported in their Process Design Kits (PDKs)

irun / OSS netlister flow


- + single netlist file in netlist directory (like spectre)
- + no need for temp libraries and shadow directories
- + faster single step irun flow & better elaboration performance
- + uses spectre CDF information
- limited support for VHDL-AMS
- no support for VHDL generics
- + no need for module views: use symbol as dummy view and include the vxl.inc file

*Source: AMS 0.18um CMOS PDK

MOTIVATION

- ASIC design is dominated by Verilog

“What is your main RTL design language?”

 

(Context: UVM webinar) (Sample size = 500 people)


*Source: www.doulos.com

VERILOG FAMILY

- Verilog
 - RTL level, verification
- VerilogA
 - Modeling of analog circuits
 - Used directly with an analog simulator!
- VerilogAMS
 - Analog and mixed signal circuits
 - Used with an mixed signal simulator!
- SystemVerilog
 - Extensions to Verilog (safer code)
 - Object-oriented paradigm (verification)

VERILOG FAMILY

 - ASIC Example
 - KTH2016-BIO3
 - Mixed-signal ASIC
 - Top-Bottom approach
 - Verilog, VerilogA, VerilogAMS



VERILOG FAMILY

- Foundry provides Verilog models for IOs


```
saul@s2424:/pkg/AMS411/verilog/h18a6
module IOPAD1V8_3 (
    // Inputs
    A, OE0, OE1, SR, PE, IE,

    // Inouts
    PAD,

    // Outputs
    Y, VDD_LOGIC0, VDD_LOGIC1

    // Supply Ring
    //VDD5V, VDD5VL, GND, SUB, SUBC, POR
    , PADA, noVDDIN
);

 input A;
input OE0;
input OE1;
input SR;
input PE;
input IE;
```




VERILOG FAMILY

- Digital blocks coded in Verilog RTL
- Synthesized, placed and routed

```


29
30 // F_PFD is the clock signal that is compared with the referen
31 // The reference clock is 500 kHz.
32 assign F_PFD = divider[5];
33
34 always @(posedge Fin, negedge Resetn)
35 begin
36 if (Resetn == 0) begin
37 divider <= 0;
38 end else begin
39 divider <= divider + 1;
40 end
41 end
42
43 // MUX 16:1
44 always @(Fsel,divider,Fin)
45 begin
46 case (Fsel)
47 4'b0000: Fout = Fin; // 32 MHz
48 4'b0001: Fout = divider[0]; // 16 MHz
49 4'b0010: Fout = divider[1]; // 8 MHz
50 4'b0011: Fout = divider[2]; // 4 MHz
51 4'b0100: Fout = divider[3]; // 2 MHz
52 4'b0101: Fout = divider[4]; // 1 MHz
53 4'b0110: Fout = divider[5]; // 500 kHz (REFERENCE FOR
54 4'b0111: Fout = divider[6]; // 250 kHz
55 4'b1000: Fout = divider[7]; // 125 kHz
56 4'b1001: Fout = divider[8]; // 62500 Hz
57 4'b1010: Fout = divider[9]; // 31250 Hz
58 4'b1011: Fout = divider[10]; // 15625 Hz
59 4'b1100: Fout = divider[11]; // 7812.5 Hz
60 4'b1101: Fout = divider[12]; // 3906.25 Hz
61 4'b1110: Fout = divider[13]; // 1953.125 Hz
62 4'b1111: Fout = divider[14]; // 976.5625 Hz
63 end
64 end

```

 

VERILOG FAMILY

- Analog blocks modeled using VerilogA

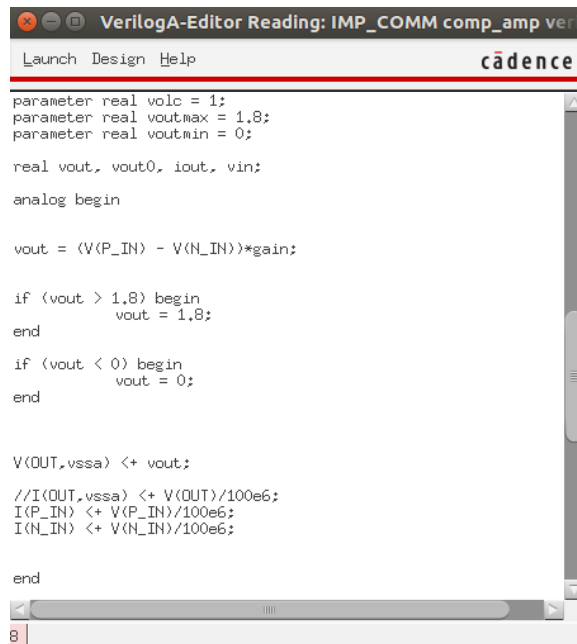

```
VerilogA-Editor Reading: IMP_COMM comp_amp ver
Launch Design Help cadence

parameter real volc = 1;
parameter real voutmax = 1.8;
parameter real voutmin = 0;

real vout, vout0, iout, vin;

analog begin


  vout = <V(P_IN) - V(N_IN)>*gain;

  if (vout > 1.8) begin
    vout = 1.8;
  end

  if (vout < 0) begin
    vout = 0;
  end

  V(OUT,vssa) <+ vout;
  //I(OUT,vssa) <+ V(OUT)/100e6;
  I(P_IN) <+ V(P_IN)/100e6;
  I(N_IN) <+ V(N_IN)/100e6;

end
```

 

VERILOG FAMILY

- Digitally controlled Analog blocks are modeled in VerilogAMS

```
VerilogAMS-Editor Reading: IMP_AN_LNA lna_gm verilogams
Launch Design Help cadence

integer analog_state = 0; // Used to communicate between dig and analog!

// Digital control block
always @(G0)
begin
    analog_state = 0;
    if (G0 == 1) begin
        analog_state = 1;
    end

    if (analog_state == 0) begin
        GM = GM0;
    end else begin
        GM = 3*GM0;
    end

    Gout=GM/Av; //Gout differential
    Gout_se = 2*Gout; //Gout single ended

end


// Analog block
analog begin

    vodif = Av*V(VIN_P,VIN_N); // Differential gain (DC)

    //Amplifier Output current
    I(IoutP,vssa) <+ (V(IoutP,vssa)-(vcm+vodif/2))*Gout_se;
    I(IoutN,vssa) <+ (V(IoutN,vssa)-(vcm+vodif/2))*Gout_se;

    //Biasing for other stages
    I(bias_CMFB) <+ -I_bias_CMFB;

end
```

 

VERILOG RTL AND SYNTHESIS EXAMPLES

- This is a short demo of Verilog RTL+ Verilog test bench code
- You can download all these examples from:
<https://github.com/saul-rodriguez/VerilogLecture>
- Recommended literature:
 - S. Brown, Z. Vranesic, “[Fundamentals of Digital Logic with Verilog Design](#)” 3rd Ed, McGRaw-Hill
 - Pong P. Chu, “FPGA Prototyping by Verilog Examples”, Wiley 2008

VERILOG RTL AND SYNTHESIS EXAMPLES

We will use these free open-source tools:

- Icarus Verilog compiler
<http://iverilog.icarus.com/>
- GTKWave waveform viewer
<http://gtkwave.sourceforge.net/>
- Yosys Open Synthesis Suite
<http://www.clifford.at/yosys/download.html>
- Geany IDE
<https://www.geany.org/>

VERILOG

- Documentation
 - // This is a short comment
 - /*This is a long Verilog comment that spans two lines */
- White spaces
 - f = f = w0; if (s == 1) f = w1;w0; if (s == 1) f = w1;
- Signals
 - type** [range] signal_name{, signal_name};

VERILOG

- Identifier names
Any character may be used (no digits at the beginning, no reserved words). Verilog is case sensitive!
- Signal Values
0 = logic value 0
1 = logic value 1
z = tri-state (high impedance)
x = unknown value
- Numbers
d = decimal
b = binary
h = hexadecimal
o = octal

VERILOG

- Example:

0

number 0

10

decimal number 10

'b10

binary number 10 = $(2)_{10}$

'h10

hex number 10 = $(16)_{10}$

4'b100

binary number 0100 = $(4)_{10}$

4'bx

unknown 4-bit value xxxx

8'b1000_0011

“_” can be inserted for readability

8'hfx

same as 8'b1111_xxxx

VERILOG

- Example:

0

number 0

10

decimal number 10

'b10

binary number 10 = $(2)_{10}$

'h10

hex number 10 = $(16)_{10}$

4'b100

binary number 0100 = $(4)_{10}$

4'bx

unknown 4-bit value xxxx

8'b1000_0011

“_” can be inserted for readability

8'hfx

same as 8'b1111_xxxx

VERILOG

- Net Types:
 - wire** x;
 - wire** Cin, AddSub;
 - wire** [3:0] S;
 - wire** [1:2] Array;
 - tri** z;
 - tri** [7:0] DataOut;
- Variable Types:
 - reg** [2:0] Count; //reg does not denote a storage element!
 - integer** k;

VERILOG

- Memories:
reg [7:0] R[3:0]; // four eight-bit variables R[0]-R[3]
reg [7:0] R[3:0][1:0]
- Operators:

Category	Examples	Bit Length
Bitwise	$\sim A$, $+A$, $-A$ $A \& B$, $A B$, $A \sim^{\wedge} B$, $A \sim^{\sim} B$	$L(A)$ $\text{MAX}(L(A), L(B))$
Logical	$!A$, $A \&\&B$, $A B$	1 bit
Reduction	$\&A$, $\sim \&A$, $ A$, $\sim A$, $\sim^{\wedge} A$, $\sim^{\sim} A$	1 bit
Relational	$A == B$, $A != B$, $A > B$, $A < B$ $A >= B$, $A <= B$ $A === B$, $A !== B$	1 bit
Arithmetic	$A + B$, $A - B$, $A * B$, A / B $A \% B$	$\text{MAX}(L(A), L(B))$
Shift	$A << B$, $A >> B$	$L(A)$
Concatenate	$\{A, \dots, B\}$	$L(A) + \dots + L(B)$
Replication	$\{B\{A\}\}$	$B * L(A)$
Condition	$A ? B : C$	$\text{MAX}(L(B), L(C))$

VERILOG

- Modules:

```
module module_name [(port name{, port name})];  
    [parameter declarations]  
    [input declarations]  
    [output declarations]  
    [inout declarations]  
    [wire or tri declarations]  
    [reg or integer declarations]  
    [function or task declarations]  
    [assign continuous assignments]  
    [initial block]  
    [always blocks]  
    [gate instantiations]  
    [module instantiations]  
endmodule
```

VERILOG

- Example full-adder 1:

```
module fulladd (Cin, x, y, s, Cout);  
  input Cin, x, y;  
  output s, Cout;  
  
  assign s = x ^ y ^ Cin;  
  assign Cout = (x & y) | (Cin & x) | (Cin & y);  
  
endmodule
```

VERILOG

- Example full-adder 2:

```
module fulladd (Cin, x, y, s, Cout);  
  input Cin, x, y;  
  output s, Cout;  
  
  assign {Cout, s} = x + y + Cin;  
  
endmodule
```

VERILOG

- Example full-adder 3:

```
module fulladd (Cin, x, y, s, Cout);  
  input Cin, x, y;  
  output s, Cout;  
  wire z1, z2, z3, z4;  
  
  and And1 (z1, x, y);  
  and And2 (z2, x, Cin);  
  and And3 (z3, y, Cin);  
  or Or1 (Cout, z1, z2, z3);  
  xor Xor1 (z4, x, y);  
  xor Xor2 (s, z4, Cin);  
  
endmodule
```


VERILOG

- Concurrent Statements

assign net_assignment{, net_assignment};

- Example:

assign Cout = (x & y) | (x & Cin) | (y & Cin);

assign S = x & y & z;

wire [1:3] A, B, C;

.

.

assign C = A & B;

wire [3:0] X, Y, S;

wire carryin, carryout;

assign {carryout, S} = X + Y + carryin;

VERILOG

- Using Parameters

```
module addern (X, Y, S, S2s);  
  parameter n = 4;  
  input [n-1:0] X, Y;  
  output [2*n-1:0] S, S2s;  
  
  assign S = X + Y,  
         S2s = {{n{X[n-1]}} , X} + {{n{Y[n-1]}} , Y};  
endmodule
```

VERILOG

- Procedural Statements (Sequential statements)

always @(sensitivity_list)

[begin]

[procedural assignment statements]

[**if-else** statements]

[**case** statements]

[**while**, **repeat**, and **for** loops]

[**task** and **function** calls]

[end]

VERILOG

- Procedural Assignments Statements
 - **Blocking Assignments** (evaluated in order at t_i)
 $S = X + Y;$
 $p = S[0];$
 - **Non-blocking Assignments** (evaluated in order but with variable values at the start of t_i)
 $S <= X + Y;$
 $p <= S[0];$
- Blocking Assignments should be used for combinational circuits
- Non-blocking Assignments should be used for sequential circuits

VERILOG

- IF-ELSE STATEMENTS

```
if (expression1) begin
    statement;
end else if (expression2) begin
    statement;
end else begin
    statement;
end
```

- Careful with default assignments, otherwise latches are implied!
- Mux2to1 Live demo

VERILOG

- CASE STATEMENT

```
case (expression)
  alternative1: begin
    statement;
  end
  alternative2: begin
    statement;
  end
  [default: begin
    statement;
  end]
endcase
```
- fulladd Live demo

VERILOG

- FOR LOOP STATEMENT

```
for (initial_index; terminal_index; increment)
  begin
    statement;
  end
```

- Example:

```
always @(X, Y, carryin)
  begin: fulladders
    integer k;
    C[0] = carryin;
    for (k = 0; k <= n-1; k = k+1) begin
      S[k] = X[k] ^ Y[k] ^ C[k];
      C[k+1] = (X[k] & Y[k]) | (C[k] & X[k]) | (C[k] & Y[k]);
    end
    carryout = C[n];
  end
```

VERILOG

- USING SUBCIRCUITS

```
module_name [#(parameter overrides)] instance_name (, .port_name (
[expression] ) {, .port_name ( [expression] )} );
```

- EXAMPLE

```
module adder4 (carryin, X, Y, S, carryout);
  input carryin;
  input [3:0] X, Y;
  output [3:0] S;
  output carryout;
  wire [3:1] C;

  fulladd stage0 (carryin, X[0], Y[0], S[0], C[1]);
  fulladd stage1 (C[1], X[1], Y[1], S[1], C[2]);
  fulladd stage2 (C[2], X[2], Y[2], S[2], C[3]);
  fulladd stage3 (.Cout(carryout), .s(S[3]), .y(Y[3]), .x(X[3]), .Cin(C[3]));
endmodule
```


VERILOG

- SEQUENTIAL CIRCUITS
 - Require procedural statements
- Gated D Latch

```
module latch (D, clk, Q);  
    input D, clk;  
    output reg Q;  
  
    always @(D, clk)  
        if (clk)  
            Q = D;  
endmodule
```

VERILOG

- D FLIP-FLOP

```
module flipflop (D, Clock, Q);  
    input D, Clock;  
    output reg Q;  
  
    always @(posedge Clock)  
        Q <= D;  
endmodule
```

- D FLIP-FLOP with asynchronous RESET (L)

```
module flipflop_ar (D, Clock, Resetn, Q);  
    input D, Clock, Resetn;  
    output reg Q;  
  
    always @(posedge Clock, negedge Resetn)  
        if (Resetn == 0)  
            Q <= 0;  
        else  
            Q <= D;  
endmodule
```

VERILOG

- D FLIP-FLOP with synchronous RESET (L)

```
module flipflop_sr (D, Clock, Resetn, Q);  
    input D, Clock, Resetn;  
    output reg Q;  
  
    always @(posedge Clock)  
        if (Resetn == 0)  
            Q <= 0;  
        else  
            Q <= D;  
endmodule
```

- LIVE DEMO: synthesis of flip-flops with synchronous and asynchronous reset

VERILOG

- Register with asynchronous clear

```
module reg4 (D, Clock, Resetn, Q);  
  input [3:0] D;  
  input Clock, Resetn;  
  output reg [3:0] Q;  
  
  always @(posedge Clock, negedge Resetn)  
    if (Resetn == 0)  
      Q <= 4'b0000;  
    else  
      Q <= D;  
endmodule
```

VERILOG

- n-bit register with asynchronous clear and enable

```
module regne (D, Clock, Resetn, E, Q);  
  parameter n = 4;  
  input [n-1:0] D;  
  input Clock, Resetn, E;  
  output reg [n-1:0] Q;  
  
  always @(posedge Clock, negedge Resetn)  
    if (Resetn == 0)  
      Q <= 0;  
    else if (E)  
      Q <= D;  
endmodule
```

- Live demo: synthesis of registers with asynch. Clear and enable

VERILOG

- Shift registers

```
module shift3 (w, Clock, Q);  
  input w, Clock;  
  output reg [1:3] Q;  
  
  always @(posedge Clock)  
  begin  
    Q[3] <= w;  
    Q[2] <= Q[3];  
    Q[1] <= Q[2];  
  end  
endmodule
```

- Live demo: synthesis of shift register

VERILOG


- Counters

```
module count4 (Clock, Resetn, E, Q);  
  input Clock, Resetn, E;  
  output reg [3:0] Q;  
  
  always @(posedge Clock, negedge Resetn)  
    if (Resetn == 0)  
      Q <= 0;  
    else if (E)  
      Q <= Q + 1;  
endmodule
```

- Live demo: simulation and synthesis of counter

VERILOG

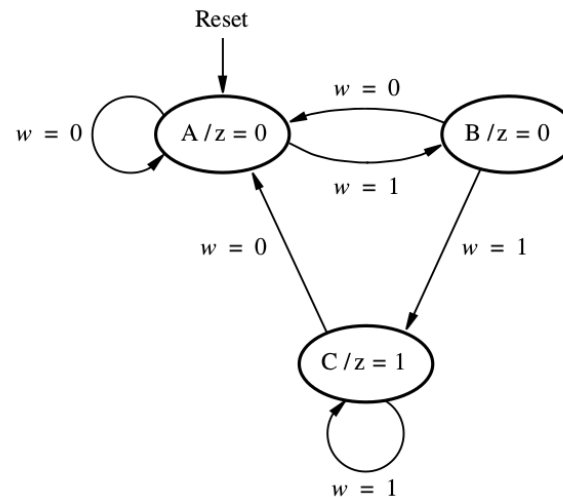- Moore-Type FSM
 - 2 always blocks:
 - 1 combinational to define next state
 - 1 sequential to assign the next state during clock edge
 - Outputs assigned in combinational block or with separate assignment statements
- EXAMPLE:



VERILOG

```
module moore (Clock, w, Resetn, z);  
  input Clock, w, Resetn;  
  output z;  
  reg [1:0] y, Y; // y = current state, Y = next state  
  parameter A = 2'b00, B = 2'b01, C = 2'b10;  
  
  always @(w, y)  
  begin  
    case (y)  
      A: if (w == 0)  Y=A;  
        else          Y=B;  
      B: if (w == 0)  Y=A;  
        else          Y=C;  
      C: if (w == 0)  Y=A;  
        else          Y=C;  
      default:        Y=2'bxx;  
    endcase  
  end
```

CODE CONTINUE IN NEXT SLIDE...

VERILOG

CONTINUATION...

```
always @(posedge Clock, negedge Resetn)
begin
    if (Resetn == 0)
        y <= A;
    else
        y <= Y;
end

assign z = (y == C); //could also be moved to top block!

endmodule
```

VERILOG

ALTERNATIVE CODE IN 1 ALWAYS BLOCK:

```
module moore (Clock, w, Resetn, z);
input Clock, w, Resetn;
output z;
reg [1:0] y;
parameter A = 2'b00, B = 2'b01, C = 2'b10;

always @(posedge Clock, negedge Resetn)
begin
    if (Resetn == 0)
        y <= A;
    else
        case (y)
            A: if (w == 0) y <= A;
               else      y <= B;
            B: if (w == 0) y <= A;
               else      y <= C;
            C: if (w == 0) y <= A;
               else      y <= C;
            default:      y <= 2'bxx;
        endcase
end

assign z = (y == C);
endmodule
```


VERILOG

```
module mealy (Clock, w, Resetn, z);  
input Clock, w, Resetn;  
output reg z;  
reg y, Y;  
parameter A = 1'b0, B = 1'b1;
```

```
always @(w, y)  
  case (y)  
    A: if (w == 0) begin  
      Y = A; z = 0;  
    end else begin  
      Y = B; z = 0;  
    end  
    B: if (w == 0) begin  
      Y = A; z = 0;  
    end else begin  
      Y = B; z = 1;  
    end  
  endcase
```

CONTINUES NEXT SLIDE...

VERILOG

CONTINUATION...

```
always @(posedge Clock, negedge Resetn)
begin
    if (Resetn == 0)
        y <= A;
    else
        y <= Y;
    end
endmodule
```

SYSTEMVERILOG

- Hardware description and Verification language HDVL
 - Combines Verilog/VHDL features with C and C++ including object oriented programming (OOP).
- Natural successor to Verilog
- Advanced tools for
 - RTL Design
 - Assertion
 - Verification
- The following is just a brief overview. For a comprehensive guide and tutorials visit:
<https://www.doulos.com>

SYSTEMVERILOG

- New data types from C:

TYPE	Description	Example
bit	user-defined size	bit [3:0] a_nibble;
byte	8 bits, signed	byte a, b;
shortint	16 bits, signed	shortint c, d;
int	32 bits, signed	int i,j;
longint	64 bits, signed	longint lword;

SYSTEMVERILOG

- New data types, same syntax as C:
typedef struct packed {
 logic [3:0] X;
 int Y;
 bit flag;
} my_type;
- Packages (VHDL, Java, C++ namespaces)
- Strings
- Classes (full OOP with single inheritance)
 - Very useful in verification

SYSTEMVERILOG

- New data types, same syntax as C:
typedef struct packed {
 logic [3:0] X;
 int Y;
 bit flag;
} my_type;
- Packages (VHDL, Java, C++ namespaces)
- Strings
- Classes (full OOP with single inheritance)

SYSTEMVERILOG

- Easier port connections
- Instantiation in Verilog:
module Design (input Clock, Reset, input [7:0] Data, output [7:0] Q);

Design DUT (Clock, Reset, Data, Q);

Design DUT (.Clock(Clock), .Reset(Reset), .Data(Data), .Q(Q));

- Instantiation in SystemVerilog:
Design DUT(.*);
Design DUT (.Clock(SysClock), .*);

SYSTEMVERILOG

- Synthesis idioms `always_comb`, `always_ff`, `always_latch`
 - Enforce checks to avoid bugs during synthesis

- Example1:

```
always_comb  
  if (sel)  
    f = x;  
  else  
    f = y;
```

- Example2:

```
always_ff @(posedge clock iff reset == 0 or posedge reset)  
  if (reset)  
    q <= 0;  
  else if (enable)  
    q++;
```

SYSTEMVERILOG

- Immediate Assertions

```
assert (A == B) $display ("OK. A equals B");  
else $error("It's gone wrong");
```

- Concurrent Assertions

```
assert property ( !(Read && Write) );  
assert property ( @(posedge Clock) Req |-> ##[1:2] Ack);
```

FINAL REMARKS

- Verilog and SystemVerilog increase in popularity
- General programming skills (C,C++,etc) are becoming very important for digital designers
- Learning Verilog after understanding VHDL is relatively easy
- To download examples:
git clone <https://github.com/saul-rodriguez/VerilogLecture>