 




# Introduction to Verilog and SystemVerilog

Saul Rodriguez



# OUTLINE


- MOTIVATION
- VERILOG FAMILY
- VERILOG RTL AND SYNTHESIS EXAMPLES
- SYSTEMVERILOG
- FINAL REMARKS

# MOTIVATION

- Digital design flows evolve towards high level languages
  - Higher productivity
  - Shorter design and verification time
  - Easy to learn
- VHDL is based on ADA
  - ADA is Strong typed, code safe
  - ADA is not very widely used
- Verilog is based on C
  - C is weak typed
  - C is the most widely spread language
  - C++, Java, C#, Objective C, Pearl, etc.
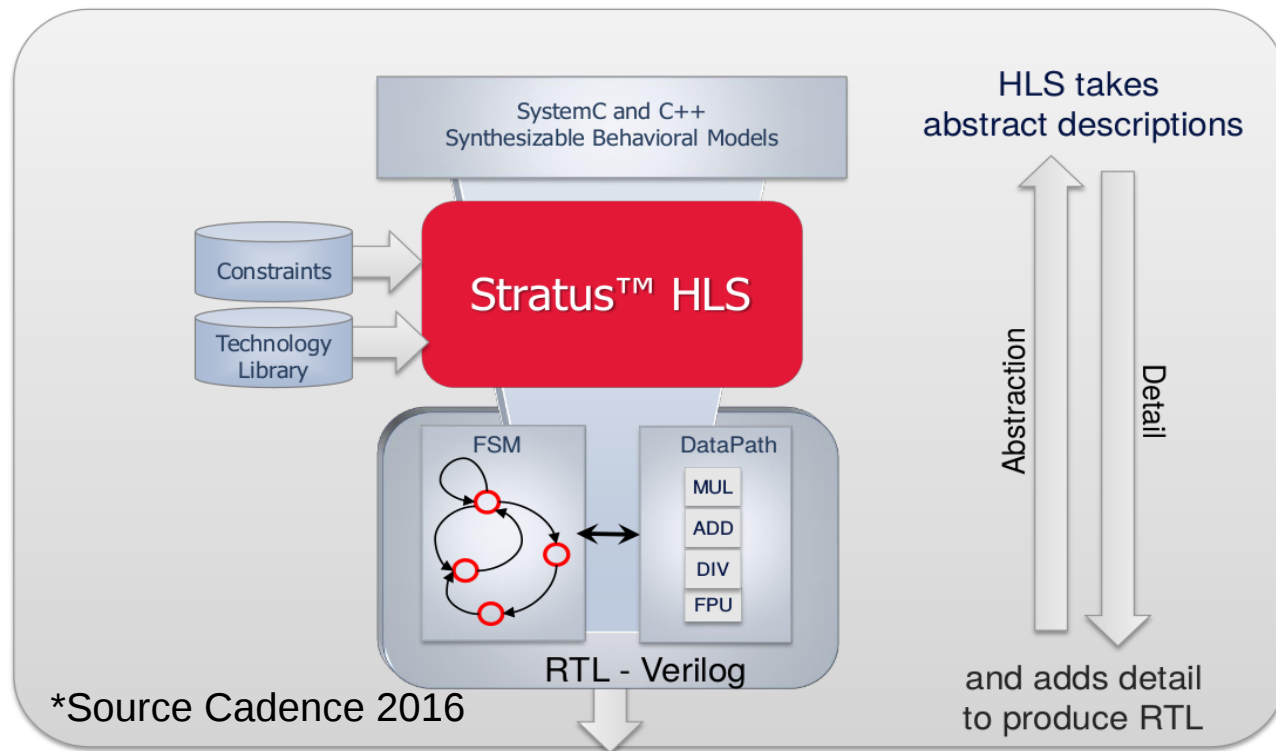
# MOTIVATION

- ASIC EDA tools are influenced by a limited number of players that decide what tool you will use.



# MOTIVATION

- ASIC Foundries decide which tools are primarily supported in their Process Design Kits (PDKs)

## irun / OSS netlister flow


- + single netlist file in netlist directory (like spectre)
- + no need for temp libraries and shadow directories
- + faster single step irun flow & better elaboration performance
- + uses spectre CDF information
- limited support for VHDL-AMS
- no support for VHDL generics
- + no need for module views: use symbol as dummy view and include the vxl.inc file

\*Source: AMS 0.18um CMOS PDK
 
# MOTIVATION

- ASIC design is dominated by Verilog

*“What is your main RTL design language?”*



(Context: UVM webinar) (Sample size = 500 people)


\*Source: [www.doulos.com](http://www.doulos.com)

# VERILOG FAMILY

- Verilog
  - RTL level, verification
- VerilogA
  - Modeling of analog circuits
  - Used directly with an analog simulator!
- VerilogAMS
  - Analog and mixed signal circuits
  - Used with an mixed signal simulator!
- SystemVerilog
  - Extensions to Verilog (safer code)
  - Object-oriented paradigm (verification)
 
# VERILOG FAMILY

- ASIC Example
  - KTH2016-BIO3
  - Mixed-signal ASIC
  - Top-Bottom approach
  - Verilog, VerilogA, VerilogAMS





# VERILOG FAMILY

- Foundry provides Verilog models for IOs


```
saul@s2424:/pkg/AMS411/verilog/h18a6
module IOPAD1V8_3 (
    // Inputs
    A, OE0, OE1, SR, PE, IE,

    // Inouts
    PAD,

    // Outputs
    Y, VDD_LOGIC0, VDD_LOGIC1

    // Supply Ring
    //VDD5V, VDD5VL, GND, SUB, SUBC, POR
    , PADA, noVDDIN
);

 input A;
input OE0;
input OE1;
input SR;
input PE;
input IE;
```




# VERILOG FAMILY

- Digital blocks coded in Verilog RTL
- Synthesized, placed and routed

```


29
30 // F_PFD is the clock signal that is compared with the referen
31 // The reference clock is 500 kHz.
32 assign F_PFD = divider[5];
33
34 always @(posedge Fin, negedge Resetn)
35 begin
36   if (Resetn == 0) begin
37     divider <= 0;
38   end else begin
39     divider <= divider + 1;
40   end
41 end
42
43 // MUX 16:1
44 always @(Fsel,divider,Fin)
45 begin
46   case (Fsel)
47     4'b0000: Fout = Fin; // 32 MHz
48     4'b0001: Fout = divider[0]; // 16 MHz
49     4'b0010: Fout = divider[1]; // 8 MHz
50     4'b0011: Fout = divider[2]; // 4 MHz
51     4'b0100: Fout = divider[3]; // 2 MHz
52     4'b0101: Fout = divider[4]; // 1 MHz
53     4'b0110: Fout = divider[5]; // 500 kHz (REFERENCE FOR
54     4'b0111: Fout = divider[6]; // 250 kHz
55     4'b1000: Fout = divider[7]; // 125 kHz
56     4'b1001: Fout = divider[8]; // 62500 Hz
57     4'b1010: Fout = divider[9]; // 31250 Hz
58     4'b1011: Fout = divider[10]; // 15625 Hz
59     4'b1100: Fout = divider[11]; // 7812 Hz
60     4'b1101: Fout = divider[12]; // 3906 Hz
61     4'b1110: Fout = divider[13]; // 1953 Hz
62     4'b1111: Fout = divider[14]; // 976 Hz
63   endcase
64 end

```

 

# VERILOG FAMILY

- Analog blocks modeled using VerilogA

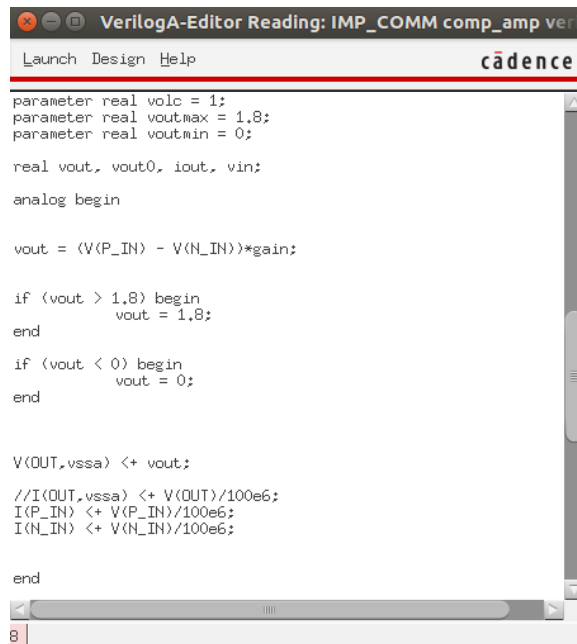

```
VerilogA-Editor Reading: IMP_COMM comp_amp ver
Launch Design Help cadence

parameter real volc = 1;
parameter real voutmax = 1.8;
parameter real voutmin = 0;

real vout, vout0, iout, vin;

analog begin


  vout = (V(P_IN) - V(N_IN))*gain;

  if (vout > 1.8) begin
    vout = 1.8;
  end

  if (vout < 0) begin
    vout = 0;
  end

  V(OUT,vssa) <+ vout;
  //I(OUT,vssa) <+ V(OUT)/100e6;
  I(P_IN) <+ V(P_IN)/100e6;
  I(N_IN) <+ V(N_IN)/100e6;

end
```

 



# VERILOG FAMILY

- Digitally controlled Analog blocks are modeled in VerilogAMS

```

VerilogAMS-Editor Reading: IMP_AN_LNA lna_gm verilogams
Launch Design Help cadence

integer analog_state = 0; // Used to communicate between dig and analog!

// Digital control block
always @(G0)
begin
    analog_state = 0;
    if (G0 == 1) begin
        analog_state = 1;
    end

    if (analog_state == 0) begin
        GM = GM0;
    end else begin
        GM = 3*GM0;
    end

    Gout=GM/Av; //Gout differential
    Gout_se = 2*Gout; //Gout single ended

end

// Analog block
analog begin


    vodif = Av*V(VIN_P,VIN_N); // Differential gain (DC)

    //Amplifier Output current
    I(IoutP,vssa) <+ (V(IoutP,vssa)-(vcm+vodif/2))*Gout_se;
    I(IoutN,vssa) <+ (V(IoutN,vssa)-(vcm+vodif/2))*Gout_se;

    //Biasing for other stages
    I(bias_CMFB) <+ -I_bias_CMFB;

end

```

 

# VERILOG RTL AND SYNTHESIS EXAMPLES

- This is a short demo of Verilog RTL+ Verilog test bench code
- You can download all these examples from:
- Recommended literature:
  - S. Brown, Z. Vranesic, “[Fundamentals of Digital Logic with Verilog Design](#)” 3<sup>rd</sup> Ed, McGraw-Hill
  - Pong P. Chu, “FPGA Prototyping by Verilog Examples”, Wiley 2008

# VERILOG RTL AND SYNTHESIS EXAMPLES

We will use these free open-source tools:

- Icarus Verilog compiler  
<http://iverilog.icarus.com/>
- GTKWave waveform viewer  
<http://gtkwave.sourceforge.net/>
- Yosys Open Synthesis Suite  
<http://www.clifford.at/yosys/download.html>
- Geany IDE  
<https://www.geany.org/>

# VERILOG

- Documentation
  - // This is a short comment
  - /\*This is a long Verilog comment that spans two lines \*/
- White spaces
  - f = f = w0; if (s == 1) f = w1;w0; if (s == 1) f = w1;
- Signals
  - type** [range] signal\_name{, signal\_name};

# VERILOG

- Identifier names  
Any character may be used (no digits at the beginning, no reserved words). Verilog is case sensitive!
- Signal Values  
0 = logic value 0  
1 = logic value 1  
z = tri-state (high impedance)  
x = unknown value
- Numbers  
d = decimal  
b = binary  
h = hexadecimal  
o = octal



# VERILOG

- Example:

0

number 0

10

decimal number 10

'b10

binary number 10 =  $(2)_{10}$

'h10

hex number 10 =  $(16)_{10}$

4'b100

binary number 0100 =  $(4)_{10}$

4'bx

unknown 4-bit value xxxx

8'b1000\_0011

“\_” can be inserted for readability

8'hfx

same as 8'b1111\_xxxx

# VERILOG

- Example:

0

number 0

10

decimal number 10

'b10

binary number 10 =  $(2)_{10}$

'h10

hex number 10 =  $(16)_{10}$

4'b100

binary number 0100 =  $(4)_{10}$

4'bx

unknown 4-bit value xxxx

8'b1000\_0011

“\_” can be inserted for readability

8'hfx

same as 8'b1111\_xxxx

# VERILOG

- Net Types:
  - wire** x;
  - wire** Cin, AddSub;
  - wire** [3:0] S;
  - wire** [1:2] Array;
  - tri** z;
  - tri** [7:0] DataOut;
- Variable Types:
  - reg** [2:0] Count; //reg does not denote a storage element!
  - integer** k;

# VERILOG

- Memories:  
`reg [7:0] R[3:0]; // four eight-bit variables R[0]-R[3]`  
`reg [7:0] R[3:0][1:0]`
- Operators:

Category	Examples	Bit Length
Bitwise	$\sim A$ , $+A$ , $-A$ $A \& B$ , $A   B$ , $A \sim^{\wedge} B$ , $A \sim^{\sim} B$	$L(A)$ $\text{MAX}(L(A), L(B))$
Logical	$!A$ , $A \&\&B$ , $A    B$	1 bit
Reduction	$\&A$ , $\sim \&A$ , $ A$ , $\sim  A$ , $\sim^{\wedge} A$ , $\sim^{\sim} A$	1 bit
Relational	$A == B$ , $A != B$ , $A > B$ , $A < B$ $A >= B$ , $A <= B$ $A === B$ , $A !== B$	1 bit
Arithmetic	$A + B$ , $A - B$ , $A * B$ , $A / B$ $A \% B$	$\text{MAX}(L(A), L(B))$
Shift	$A << B$ , $A >> B$	$L(A)$
Concatenate	$\{A, \dots, B\}$	$L(A) + \dots + L(B)$
Replication	$\{B\{A\}\}$	$B * L(A)$
Condition	$A ? B : C$	$\text{MAX}(L(B), L(C))$

# VERILOG

- Modules:

```
module module_name [(port name{, port name})];  
    [parameter declarations]  
    [input declarations]  
    [output declarations]  
    [inout declarations]  
    [wire or tri declarations]  
    [reg or integer declarations]  
    [function or task declarations]  
    [assign continuous assignments]  
    [initial block]  
    [always blocks]  
    [gate instantiations]  
    [module instantiations]  
endmodule
```

# VERILOG

- Example full-adder 1:

```
module fulladd (Cin, x, y, s, Cout);  
  input Cin, x, y;  
  output s, Cout;  
  
  assign s = x ^ y ^ Cin;  
  assign Cout = (x & y) | (Cin & x) | (Cin & y);  
  
endmodule
```

# VERILOG

- Example full-adder 2:

```
module fulladd (Cin, x, y, s, Cout);  
  input Cin, x, y;  
  output s, Cout;  
  
  assign {Cout, s} = x + y + Cin;  
  
endmodule
```

# VERILOG

- Example full-adder 3:

```
module fulladd (Cin, x, y, s, Cout);  
  input Cin, x, y;  
  output s, Cout;  
  wire z1, z2, z3, z4;  
  
  and And1 (z1, x, y);  
  and And2 (z2, x, Cin);  
  and And3 (z3, y, Cin);  
  or Or1 (Cout, z1, z2, z3);  
  xor Xor1 (z4, x, y);  
  xor Xor2 (s, z4, Cin);  
  
endmodule
```



# VERILOG

- Concurrent Statements

**assign** net\_assignment{, net\_assignment};

- Example:

**assign** Cout = (x & y) | (x & Cin) | (y & Cin);

**assign** S = x & y & z;

**wire** [1:3] A, B, C;

.

.

**assign** C = A & B;

**wire** [3:0] X, Y, S;

**wire** carryin, carryout;

**assign** {carryout, S} = X + Y + carryin;

# VERILOG

- Using Parameters

```
module addern (X, Y, S, S2s);  
  parameter n = 4;  
  input [n-1:0] X, Y;  
  output [2*n-1:0] S, S2s;  
  
  assign S = X + Y,  
         S2s = {{n{X[n-1]}} , X} + {{n{Y[n-1]}} , Y};  
endmodule
```

# VERILOG

- Procedural Statements (Sequential statements)

**always** @(sensitivity\_list)

**[begin]**

[procedural assignment statements]

[**if-else** statements]

[**case** statements]

[**while**, **repeat**, and **for** loops]

[**task** and **function** calls]

**[end]**

# VERILOG

- Procedural Assignments Statements
  - **Blocking Assignments** (evaluated in order at  $t_i$ )  
 $S = X + Y;$   
 $p = S[0];$
  - **Non-blocking Assignments** (evaluated in order but with variable values at the start of  $t_i$ )  
 $S <= X + Y;$   
 $p <= S[0];$
- Blocking Assignments should be used for combinational circuits
- Non-blocking Assignments should be used for sequential circuits

# VERILOG

- IF-ELSE STATEMENTS

```
if (expression1) begin
    statement;
end else if (expression2) begin
    statement;
end else begin
    statement;
end
```

- Careful with default assignments, otherwise latches are implied!
- Mux2to1 Live demo

# VERILOG

- CASE STATEMENT

```
case (expression)
  alternative1: begin
    statement;
  end
  alternative2: begin
    statement;
  end
  [default: begin
    statement;
  end]
endcase
```
- fulladd Live demo

# VERILOG

- FOR LOOP STATEMENT

```
for (initial_index; terminal_index; increment)
  begin
    statement;
  end
```

- Example:

```
always @(X, Y, carryin)
  begin: fulladders
    integer k;
    C[0] = carryin;
    for (k = 0; k <= n-1; k = k+1) begin
      S[k] = X[k] ^ Y[k] ^ C[k];
      C[k+1] = (X[k] & Y[k]) | (C[k] & X[k]) | (C[k] & Y[k]);
    end
    carryout = C[n];
  end
```

# VERILOG

- USING SUBCIRCUITS

```
module_name [#(parameter overrides)] instance_name (, .port_name (
[expression] ) {, .port_name ( [expression] )} );
```

- EXAMPLE

```
module adder4 (carryin, X, Y, S, carryout);
  input carryin;
  input [3:0] X, Y;
  output [3:0] S;
  output carryout;
  wire [3:1] C;

  fulladd stage0 (carryin, X[0], Y[0], S[0], C[1]);
  fulladd stage1 (C[1], X[1], Y[1], S[1], C[2]);
  fulladd stage2 (C[2], X[2], Y[2], S[2], C[3]);
  fulladd stage3 (.Cout(carryout), .s(S[3]), .y(Y[3]), .x(X[3]), .Cin(C[3]));
endmodule
```



# VERILOG

- SEQUENTIAL CIRCUITS
  - Require procedural statements
- Gated D Latch

```
module latch (D, clk, Q);  
    input D, clk;  
    output reg Q;  
  
    always @(D, clk)  
        if (clk)  
            Q = D;  
endmodule
```

# VERILOG

- D FLIP-FLOP

```
module flipflop (D, Clock, Q);  
    input D, Clock;  
    output reg Q;  
  
    always @(posedge Clock)  
        Q <= D;  
endmodule
```

- D FLIP-FLOP with asynchronous RESET (L)

```
module flipflop_ar (D, Clock, Resetn, Q);  
    input D, Clock, Resetn;  
    output reg Q;  
  
    always @(posedge Clock, negedge Resetn)  
        if (Resetn == 0)  
            Q <= 0;  
        else  
            Q <= D;  
endmodule
```

# VERILOG

- D FLIP-FLOP with synchronous RESET (L)

```
module flipflop_sr (D, Clock, Resetn, Q);  
    input D, Clock, Resetn;  
    output reg Q;  
  
    always @(posedge Clock)  
        if (Resetn == 0)  
            Q <= 0;  
        else  
            Q <= D;  
endmodule
```

- LIVE DEMO: synthesis of flip-flops with synchronous and asynchronous reset

# VERILOG

- Register with asynchronous clear

```
module reg4 (D, Clock, Resetn, Q);  
  input [3:0] D;  
  input Clock, Resetn;  
  output reg [3:0] Q;  
  
  always @(posedge Clock, negedge Resetn)  
    if (Resetn == 0)  
      Q <= 4'b0000;  
    else  
      Q <= D;  
endmodule
```

# VERILOG

- n-bit register with asynchronous clear and enable

```
module regne (D, Clock, Resetn, E, Q);  
  parameter n = 4;  
  input [n-1:0] D;  
  input Clock, Resetn, E;  
  output reg [n-1:0] Q;  
  
  always @(posedge Clock, negedge Resetn)  
    if (Resetn == 0)  
      Q <= 0;  
    else if (E)  
      Q <= D;  
endmodule
```

- Live demo: synthesis of registers with asynch. Clear and enable

# VERILOG

- Shift registers

```
module shift3 (w, Clock, Q);  
  input w, Clock;  
  output reg [1:3] Q;  
  
  always @(posedge Clock)  
  begin  
    Q[3] <= w;  
    Q[2] <= Q[3];  
    Q[1] <= Q[2];  
  end  
endmodule
```

- Live demo: synthesis of shift register

# VERILOG


- Counters

```
module count4 (Clock, Resetn, E, Q);  
  input Clock, Resetn, E;  
  output reg [3:0] Q;  
  
  always @(posedge Clock, negedge Resetn)  
    if (Resetn == 0)  
      Q <= 0;  
    else if (E)  
      Q <= Q + 1;  
endmodule
```

- Live demo: simulation and synthesis of counter
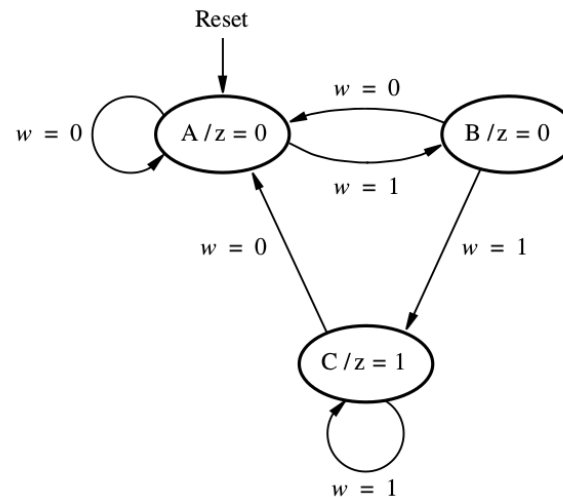
# VERILOG

- Moore-Type FSM
  - 2 always blocks:
    - 1 combinational to define next state
    - 1 sequential to assign the next state during clock edge
  - Outputs assigned in combinational block or with separate assignment statements
- EXAMPLE:





# VERILOG

```
module moore (Clock, w, Resetn, z);  
  input Clock, w, Resetn;  
  output z;  
  reg [1:0] y, Y; // y = current state, Y = next state  
  parameter A = 2'b00, B = 2'b01, C = 2'b10;  
  
  always @(w, y)  
  begin  
    case (y)  
      A: if (w == 0)  Y=A;  
        else         Y=B;  
      B: if (w == 0)  Y=A;  
        else         Y=C;  
      C: if (w == 0)  Y=A;  
        else         Y=C;  
      default:       Y=2'bxx;  
    endcase  
  end
```

**CODE CONTINUE IN NEXT SLIDE...**

# VERILOG

## CONTINUATION...

```
always @(posedge Clock, negedge Resetn)
begin
    if (Resetn == 0)
        y <= A;
    else
        y <= Y;
end

assign z = (y == C); //could also be moved to top block!

endmodule
```

# VERILOG

## ALTERNATIVE CODE IN 1 ALWAYS BLOCK:

```
module moore (Clock, w, Resetn, z);  
input Clock, w, Resetn;  
output z;  
reg [1:0] y;  
parameter A = 2'b00, B = 2'b01, C = 2'b10;  
  
always @(posedge Clock, negedge Resetn)  
begin  
    if (Resetn == 0)  
        y <= A;  
    else  
        case (y)  
            A: if (w == 0) y <= A;  
               else      y <= B;  
            B: if (w == 0) y <= A;  
               else      y <= C;  
            C: if (w == 0) y <= A;  
               else      y <= C;  
            default:      y <= 2'bxx;  
        endcase  
    end  
  
    assign z = (y == C);  
endmodule
```

- 
- Diagram illustrating a two-state Markov chain with states A and B. The transitions are labeled with  $w$  and  $z$  values:
- State A has a self-loop labeled  $w = 0 / z = 0$ .
  - State A transitions to State B labeled  $w = 1 / z = 0$ .
  - State B transitions back to State A labeled  $w = 0 / z = 0$ .
  - State B has a self-loop labeled  $w = 1 / z = 1$ .
  - A "Reset" arrow points to State A.

# VERILOG

```
module mealy (Clock, w, Resetn, z);  
input Clock, w, Resetn;  
output reg z;  
reg y, Y;  
parameter A = 1'b0, B = 1'b1;
```

```
always @(w, y)  
  case (y)  
    A: if (w == 0) begin  
      Y = A; z = 0;  
    end else begin  
      Y = B; z = 0;  
    end  
    B: if (w == 0) begin  
      Y = A; z = 0;  
    end else begin  
      Y = B; z = 1;  
    end  
  endcase
```

CONTINUES NEXT SLIDE...

# VERILOG

## CONTINUATION...

```
always @(posedge Clock, negedge Resetn)
begin
    if (Resetn == 0)
        y <= A;
    else
        y <= Y;
    end
endmodule
```

# SYSTEMVERILOG

- Hardware description and Verification language HDVL
  - Combines Verilog/VHDL features with C and C++ including object oriented programming (OOP).
- Natural successor to Verilog
- Advanced tools for
  - RTL Design
  - Assertion
  - Verification
- The following is just a brief overview. For a comprehensive guide and tutorials visit:  
<https://www.doulos.com>

# SYSTEMVERILOG

- New data types from C:

<b>TYPE</b>	<b>Description</b>	<b>Example</b>
bit	user-defined size	bit [3:0] a_nibble;
byte	8 bits, signed	byte a, b;
shortint	16 bits, signed	shortint c, d;
int	32 bits, signed	int i,j;
longint	64 bits, signed	longint lword;



# SYSTEMVERILOG

- New data types, same syntax as C:  
**typedef struct packed {**  
    **logic** [3:0] X;  
    **int** Y;  
    **bit** flag;  
} my\_type;
- Packages (VHDL, Java, C++ namespaces)
- Strings
- Classes (full OOP with single inheritance)
  - Very useful in verification

# SYSTEMVERILOG

- New data types, same syntax as C:  
**typedef struct packed {**  
    **logic** [3:0] X;  
    **int** Y;  
    **bit** flag;  
} my\_type;
- Packages (VHDL, Java, C++ namespaces)
- Strings
- Classes (full OOP with single inheritance)

# SYSTEMVERILOG

- Easier port connections
- Instantiation in Verilog:  
**module** Design (input Clock, Reset, input [7:0] Data, output [7:0] Q);

Design DUT ( Clock, Reset, Data, Q );

Design DUT ( .Clock(Clock), .Reset(Reset), .Data(Data), .Q(Q) );

- Instantiation in SystemVerilog:  
Design DUT(.\*);  
Design DUT ( .Clock(SysClock), .\* );

# SYSTEMVERILOG

- Synthesis idioms `always_comb`, `always_ff`, `always_latch`
  - Enforce checks to avoid bugs during synthesis

- Example1:

```
always_comb  
  if (sel)  
    f = x;  
  else  
    f = y;
```

- Example2:

```
always_ff @(posedge clock iff reset == 0 or posedge reset)  
  if (reset)  
    q <= 0;  
  else if (enable)  
    q++;
```

# SYSTEMVERILOG

- Immediate Assertions

```
assert (A == B) $display ("OK. A equals B");  
else $error("It's gone wrong");
```

- Concurrent Assertions

```
assert property ( !(Read && Write) );  
assert property ( @(posedge Clock) Req |-> ##[1:2] Ack);
```



# FINAL REMARKS

- Verilog and SystemVerilog increase in popularity
- General programming skills (C,C++,etc) are becoming very important for digital designers
- Learning Verilog after understanding VHDL is relatively easy